

The output voltage  $V_o$  can be changed by varying the feedback factor  $\beta$ . The emitter follower  $Q1$  is used to provide current gain, because the current delivered by the amplifier  $A_V$  usually is not sufficient. The dc collector voltage required by the error amplifier  $A_V$  is obtained from the unregulated voltage.

**Stabilization** Since the output dc voltage  $V_o$  depends on the input unregulated dc voltage  $V_i$ , load current  $I_L$ , and temperature  $T$ , then the change  $\Delta V_o$  in output voltage of a power supply can be expressed as follows:

$$\Delta V_o = \frac{\partial V_o}{\partial V_i} \Delta V_i + \frac{\partial V_o}{\partial I_L} \Delta I_L + \frac{\partial V_o}{\partial T} \Delta T$$

or

$$\Delta V_o = S_V \Delta V_i + R_o \Delta I_L + S_T \Delta T \quad (18-50)$$

where the three coefficients are defined as

$$\text{Input regulation factor:} \quad S_V = \left. \frac{\Delta V_o}{\Delta V_i} \right|_{\substack{\Delta I_L=0 \\ \Delta T=0}} \quad (18-51)$$

$$\text{Output resistance:} \quad R_o = \left. \frac{\Delta V_o}{\Delta I_L} \right|_{\substack{\Delta V_i=0 \\ \Delta T=0}} \quad (18-52)$$

$$\text{Temperature coefficient:} \quad S_T = \left. \frac{\Delta V_o}{\Delta T} \right|_{\substack{\Delta V_i=0 \\ \Delta I_L=0}} \quad (18-53)$$

The smaller the value of the three coefficients, the better the regulation of the power supply. The input-voltage change  $\Delta V_i$  may be due to a change in ac line voltage or may be ripple because of inadequate filtering.

## 18-10 SERIES VOLTAGE REGULATOR

The physical reason for the improvement in voltage regulation with the circuit of Fig. 18-16 lies in the fact that a large fraction of the *increase* in input voltage appears across the pass element, so that the output voltage tries to remain constant. If the input increases, the output must also increase (but to a much smaller extent), because it is this increase in output that acts to bias the pass transistor toward less current. This stabilization is demonstrated with reference to Fig. 18-17 where  $Q2$  is the comparison amplifier designated  $A_V$  in Fig. 18-16, and where the battery  $V_R$  is replaced by the breakdown diode  $D$ . Here a fraction of the output voltage  $\beta V_o$  is compared with the reference voltage  $V_R$ . The difference  $\beta V_o - V_R$  is amplified by  $Q2$ . If the input voltage increases by  $\Delta V_i$  (say, because the power-line voltage increases), then  $V_o$  need increase only slightly, and yet  $Q2$  may cause a large current change in  $R_3$ . Thus it is possible for almost all of  $\Delta V_i$  to appear across  $R_3$  (and since the base-to-emitter voltage is small, also across  $Q1$ ) and for  $V_o$  to remain essentially constant. These considerations are now made more quantitative.

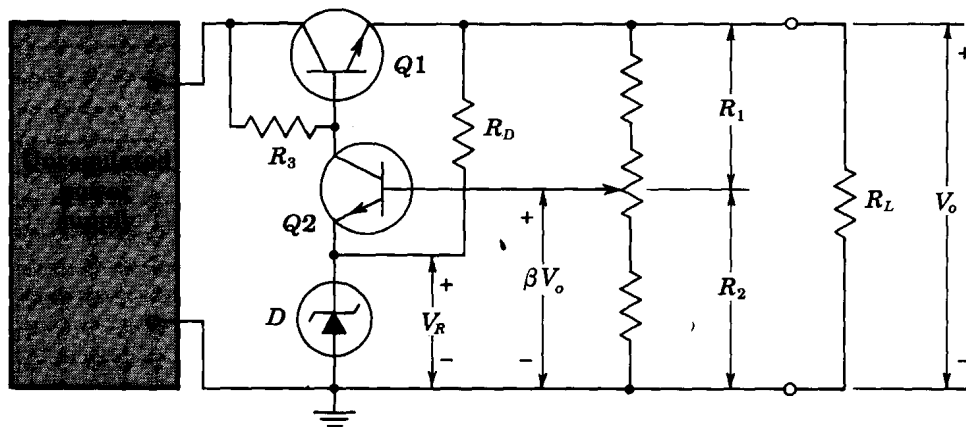


Fig. 18-17 A semiconductor-regulated power supply. The series pass element or series regulator is  $Q1$ , the difference amplifier is  $Q2$ , and the reference avalanche diode is  $D$ .

**Simplified Analysis** From Fig. 18-17 the output dc voltage  $V_o$  is given by

$$V_o = V_R + V_{BE2} + \frac{R_1}{R_1 + R_2} V_o$$

or using Eq. (18-48) for  $\beta$

$$V_o = (V_R + V_{BE2}) \left( 1 + \frac{R_1}{R_2} \right) = (V_R + V_{BE2}) / \beta \quad (18-54)$$

Hence a convenient method for changing the output is to adjust the ratio  $R_1/R_2$  by means of a resistance divider as indicated in Fig. 18-17.

An approximate expression for  $S_V$  (sufficiently accurate for most applications) is obtained as follows: The input-voltage change  $v_i$  is very much larger than the output change  $v_o$ . Also, by the definition of Eq. (18-51),  $\Delta I_L = 0$ , and to a first approximation we can neglect the ac voltage drop across  $r_o$ . Hence  $\Delta V_i = v_i$  appears as shown in Fig. 18-18. Neglecting the

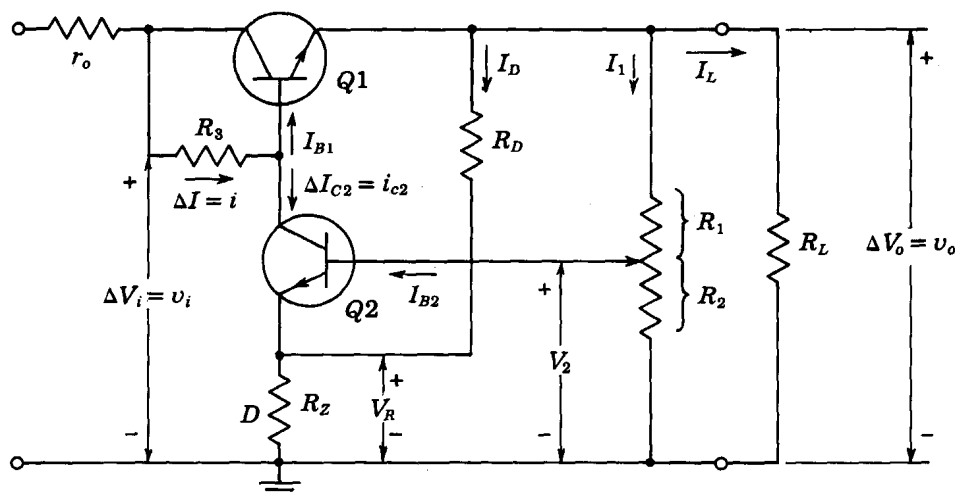


Fig. 18-18 Analysis of the series-regulated power supply.

small change in base-to-emitter voltage of Q1, the current change  $\Delta I = i$  in  $R_3$  is given by

$$i = \frac{v_i - v_o}{R_3} \approx \frac{v_i}{R_3} \quad (18-55)$$

Since  $R_L$  is fixed, constant output voltage requires that  $I_L$ , and hence  $I_{B1}$ , remain constant. Hence, for constant  $I_{B1}$ ,

$$i = \Delta I_{C2} = i_{c2} \quad (18-56)$$

In Prob. 18-23 we find, for small values of  $R_3$ , that  $i_{c2} = G_m v_o$  where

$$G_m = h_{fe2} \frac{R_2}{R_1 + R_2} \frac{1}{(R_1 || R_2) + h_{ie2} + (1 + h_{fe2}) R_Z} \quad (18-57)$$

where  $R_Z$  is the dynamic resistance of the Zener diode. Using Eqs. (18-55) to (18-57), we find, since  $v_i \approx i_{c2} R_3$ ,

$$S_V = \frac{v_o}{v_i} = \frac{1}{G_m R_3} \quad (18-58)$$

In Prob. 18-24 the output resistance  $R_o$  of the circuit of Fig. 18-18 is found to be

$$R_o \approx \frac{r_o + (R_3 + h_{ie1})/(1 + h_{fe1})}{1 + G_m(R_3 + r_o)} \quad (18-59)$$

where  $G_m \equiv i_{c2}/v_o$  is obtained from Eq. (18-57). A design procedure is indicated in the following illustrative example.

---

**EXAMPLE** (a) Design a series-regulated power supply to provide a nominal output voltage of 25 V and supply load current  $I_L \leq 1$  A. The unregulated power supply has the following specifications:  $V_i = 50 \pm 5$  V and  $r_o = 10 \Omega$ . (b) Find the input regulation factor  $S_V$ . (c) Find the output resistance  $R_o$ . (d) Compute the change in output voltage  $\Delta V_o$  due to input-voltage changes of  $\pm 5$  V and load current  $I_L$  variation from zero to 1 A.

**Solution** a. Select a silicon reference diode with  $V_R \approx V_o/2$ . Two 1N755 diodes in series provide  $V_R = 7.5 + 7.5 = 15$  V and  $R_Z = 12 \Omega$  at  $I_Z = 20$  mA. Refer to Figs. 18-18 and 18-19. Choose  $I_{C2} \approx I_{E2} = 10$  mA. The Texas Instruments 2N930 silicon transistor can provide the collector current of 10 mA. For this transistor the manufacturer specifies  $I_{C,\max} = 30$  mA and  $V_{CE,\max} = 45$  V.

At  $I_{C2} = 10$  mA, the following parameters were measured:

$$h_{FE2} = 220 \quad h_{fe2} = 200 \quad h_{ie2} = 800 \Omega$$

Choose  $I_D = 10$  mA, so that D1, D2, operate at  $I_z = 10 + 10 = 20$  mA. Then

$$R_D = \frac{V_o - V_R}{I_D} = \frac{25 - 15}{10} = 1 \text{ K}$$

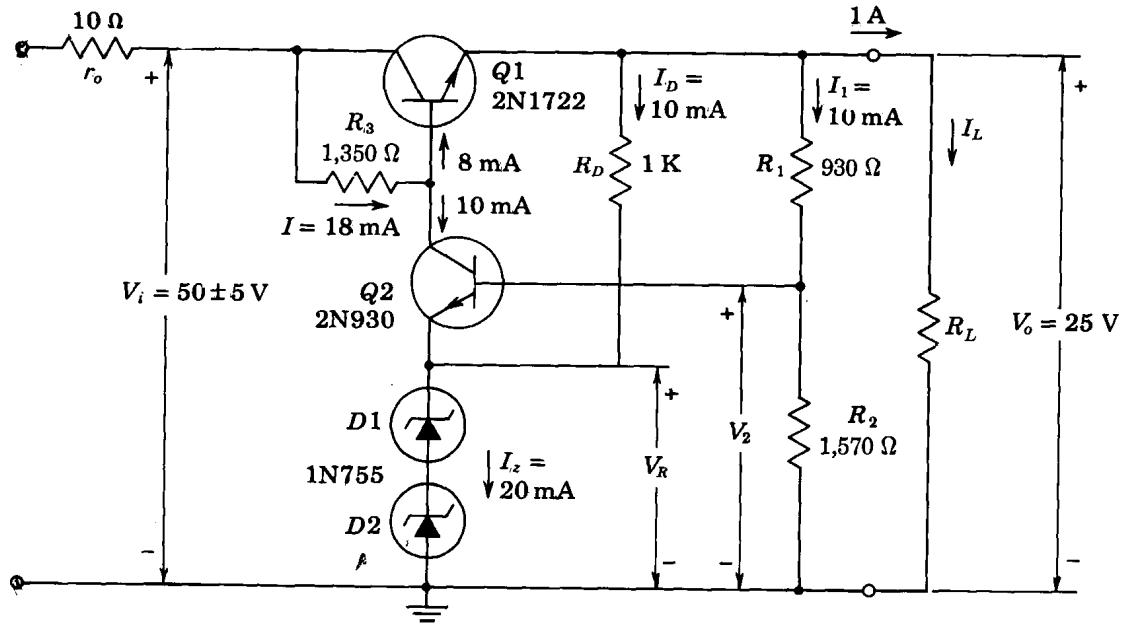


Fig. 18-19 The series regulator discussed in the example.

The ratio  $R_1/R_2$  may be found from Eq. (18-54). Each resistor is determined as follows:

$$I_{B2} = \frac{I_{C2}}{h_{FE2}} = \frac{10\text{ mA}}{220} = 45\ \mu\text{A}$$

Since we require  $I_1 \gg I_{B2}$ , we select  $I_1 = 10\text{ mA}$ ; then, since  $V_{BE} = 0.7\text{ V}$ ,

$$V_2 = V_{BE2} + V_R = 15.7\text{ V}$$

$$R_1 = \frac{V_o - V_2}{I_1} = \frac{25 - 15.7}{10 \times 10^{-3}} = 930\ \Omega$$

$$R_2 \approx \frac{V_2}{I_1} = \frac{15.7}{10 \times 10^{-3}} = 1,570\ \Omega$$

If we select the Texas Instruments 2N1722 silicon power transistor for  $Q_1$ , we measure at  $I_{C1} = 1\text{ A}$  the following parameters:

$$h_{FE1} = 125 \quad h_{fe1} = 100 \quad h_{ie1} = 20\ \Omega$$

We thus have

$$I_{B1} = \frac{I_L + I_1 + I_D}{h_{FE1}} = \frac{1,000 + 10 + 10}{125} \approx 8\text{ mA}$$

The current  $I$  through resistor  $R_3$  is  $I = I_{B1} + I_{C2} = 8 + 10 = 18\text{ mA}$ . The value for  $R_3$  corresponding to  $V_i = 45$  and to  $I_L = 1\text{ A}$  is given by

$$R_3 = \frac{V_i - (V_{BE1} + V_o)}{I} = \frac{50 - 25.7}{18 \times 10^{-3}} = 1,350\ \Omega$$

The complete circuit is shown in Fig. 18-19.

b. From Eq. (18-58) we find

$$S_V = \frac{2.50}{1.57} \times \frac{584 + 800 + (201)(12)}{(200)(1,350)} = 0.022$$

c. The output resistance is found from Eqs. (18-58) and (18-59). Since

$$G_m = \frac{1}{S_V R_3} = \frac{1}{0.022 \times 1,350} = 0.033$$

$$R_o = \frac{10 + (1,350 + 20)/101}{1 + (0.033)(1,350 + 10)} = 0.51 \Omega$$

d. The net change in output voltage, assuming constant temperature, is obtained using Eq. (18-50):

$$\Delta V_o = S_V \Delta V_i + R_o \Delta I_L = 0.022 \times 10 + 0.51 \times 1 = 0.22 + 0.51 = 0.73 \text{ V}$$

The circuit designed in this example was built in the laboratory, and excellent agreement between measured and calculated values was obtained.

Very often it is necessary to design a power supply with much smaller value for  $S_V$ . From Eq. (18-58) we see that  $S_V$  can be improved if  $R_3$  is increased. Since  $R_3 \approx (V_i - V_o)/I$ , we can increase  $R_3$  by decreasing  $I$ . The current  $I$  can be decreased by using a Darlington pair (Fig. 8-29) for  $Q1$ . For even greater improvement in  $S_V$ ,  $R_3$  is replaced by a constant-current source (so that  $R_3 \rightarrow \infty$ ), as shown in Fig. 18-20 (see also Sec. 15-3). For this circuit, which incorporates a Darlington pair, values of  $S_V = 0.00014$  and  $R_o = 0.1 \Omega$  have been obtained.<sup>9</sup> The constant-current source in Fig. 18-20 is often called a *transistor preregulator*. Other types of preregulators (Prob. 18-28) are possible.<sup>9</sup> The  $0.01\text{-}\mu\text{F}$  capacitor in Fig. 18-20 is added to prevent high-frequency oscillation.

**Practical Considerations** The maximum dc load current of the power supply shown in Fig. 18-18 is restricted by the maximum allowable collector current of the series transistor. The difference between the output and input voltages of the regulator is applied across  $Q1$ , and thus the maximum allowable  $V_{CE}$  for a given  $Q1$  and specified output voltage determines the maximum input voltage to the regulator. The product of the load current and  $V_{CE}$  is approximately equal to the power dissipated in the pass transistor. Consequently, the maximum allowable power dissipated in the series transistor further limits the combination of load current and input voltage of the regulator.

The reverse saturation current  $I_{CO1}$  of  $Q1$  in Fig. 18-18 plays an important role in determining the minimum load of the regulator. If  $I_{B1} = 0$ , then

$$I_{C1} = -I_{E1} = I_{CO1}(1 + h_{FE1})$$

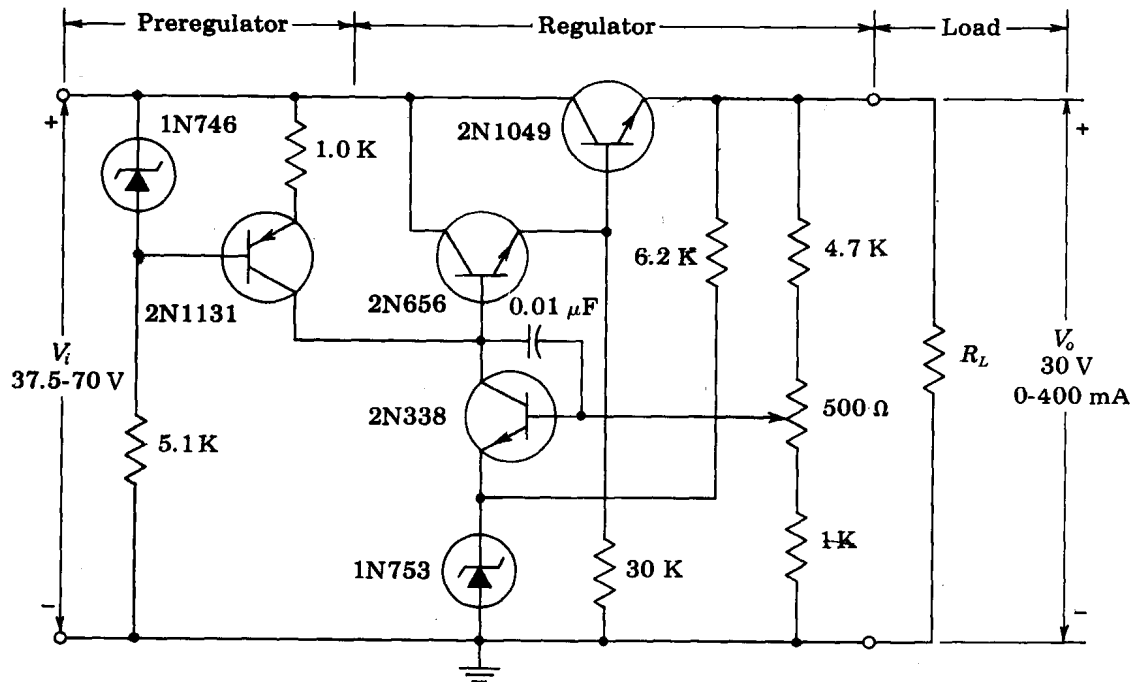


Fig. 18-20 Typical series regulator using preregulator and Darlington pair. (Courtesy of Texas Instruments, Inc.)

Hence, if the emitter current of  $Q_1$  ( $I_L + I_D + I_1$ ) falls below  $I_{CO1}(1 + h_{FE1})$ , then  $V_{CE1}$  cannot be controlled by  $I_{B1}$ , and the regulator cannot function properly. We thus see that, at high temperatures, where  $I_{CO}$  and  $h_{FE}$  are high, the regulator may fail when the load current falls below a certain minimum level. Various techniques have been proposed<sup>10</sup> to reduce this minimum-load restriction due to  $I_{CO}$ . The 30-K resistor in Fig. 18-20 is added to allow operation at low load currents.

A power supply must be protected further from the possibility of damage through overload. In simple circuits protection is provided by using a fusible element in series with  $r_o$ . In more sophisticated equipment the series transistor is such that it can permit operation at any voltage from zero to the maximum output voltage. In case of an overload or short circuit, the circuit of Fig. 18-21 can provide protection. Here the diodes  $D_1$ ,  $D_2$  are nonconducting until the voltage drop across the sensing resistor  $R_S$  exceeds their forward threshold voltage  $V_\gamma$ . Thus, in the case of a short circuit, the current  $I_S$  would increase only up to a limiting point determined by

$$I_S = \frac{V_{\gamma 1} + V_{\gamma 2} - V_{BE1}}{R_S}$$

Under short-circuit conditions the load current would be, approximately,

$$I_L \approx \frac{V_i}{R_3} + \frac{V_{\gamma 1} + V_{\gamma 2} - V_{BE1}}{R_S} \quad (18-60)$$

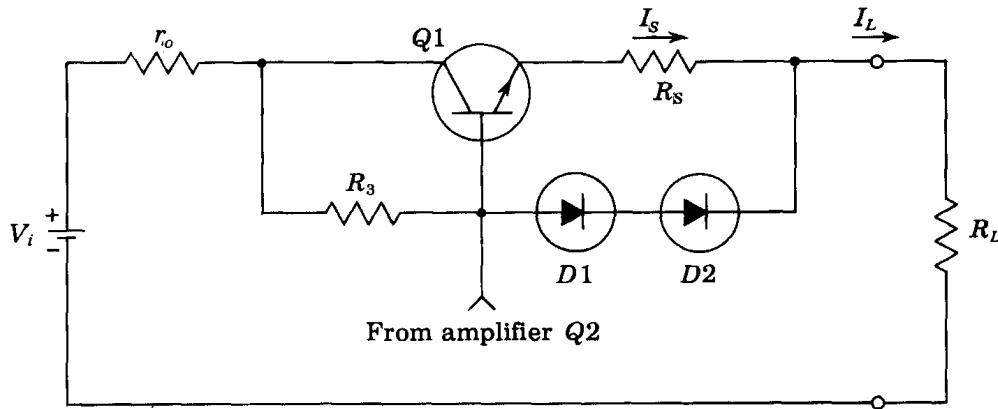


Fig. 18-21 Short-circuit overload-protection circuit.

Finally, an important practical consideration is the variation in output voltage with temperature. From Eq. (18-54) we see that, approximately,

$$\frac{\Delta V_o}{\Delta T} \approx \left( \frac{\Delta V_R}{\Delta T} + \frac{\Delta V_{BE2}}{\Delta T} \right) \left( 1 + \frac{R_1}{R_2} \right) \quad (18-61)$$

Thus cancellation of temperature coefficients between the reference diode  $D1$  and the transistor  $Q2$  can result in a very low  $\Delta V_o/\Delta T$ . The GE reference amplifiers RA-1, RA-2, and RA-3 have been designed for this purpose. They are integrated devices composed of a reference diode and  $n$ - $p$ - $n$  transistor in a single chip. Typical temperature coefficients for these units are better than  $\pm 0.002$  percent/ $^{\circ}\text{C}$ .