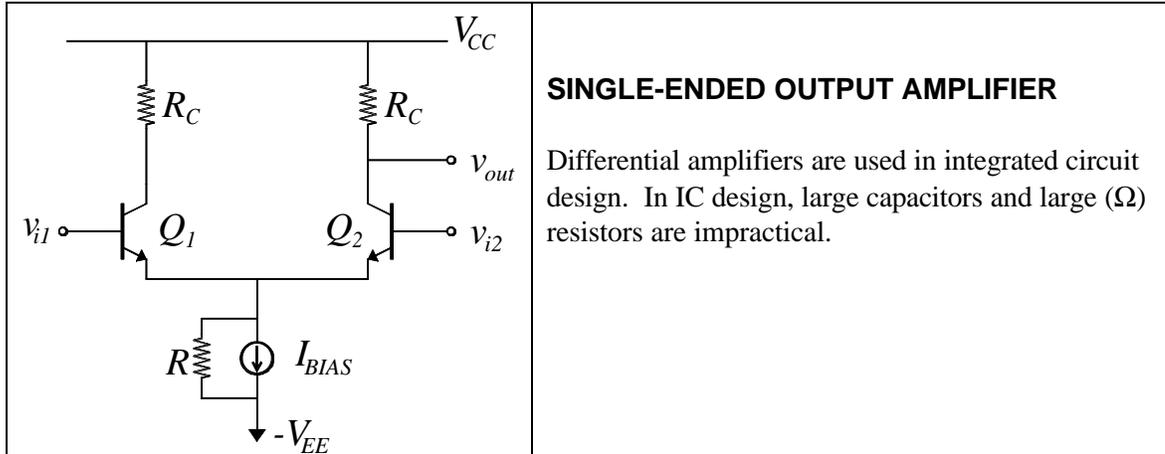



# DIFFERENTIAL AMPLIFIER, SINGLE-ENDED OUTPUT

Analysis of a symmetrical differential single-ended output amplifier

## THE CIRCUIT



## DC ANALYSIS

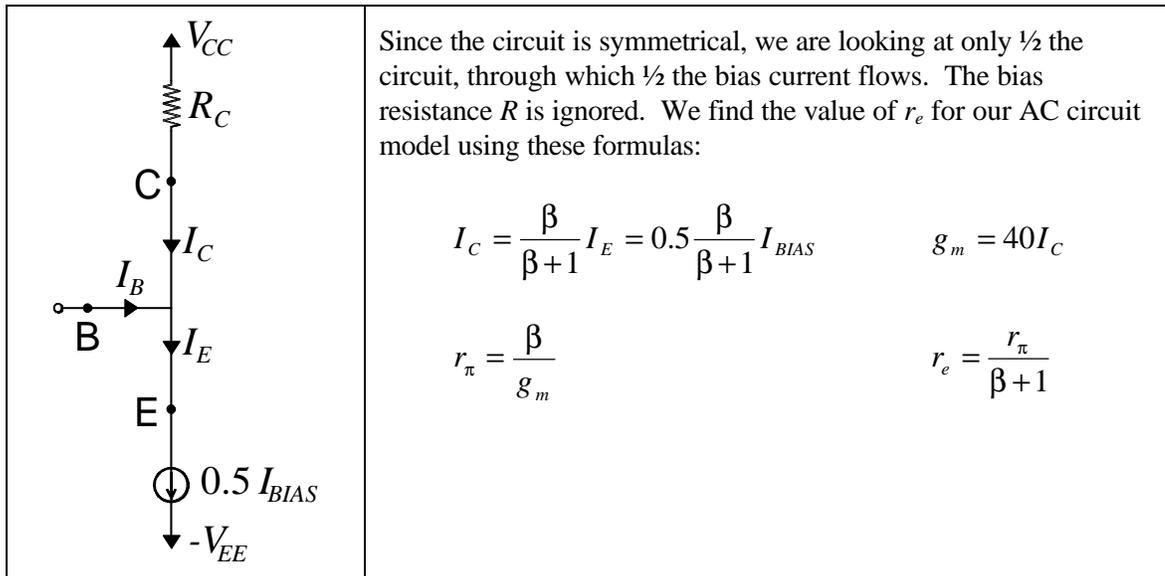

## AC ANALYSIS

For the AC analysis, we divide the input signals  $v_{i1}$  and  $v_{i2}$  into differential and common-mode components. The inputs are written as

$v_{i1} = v_{icm} + \frac{v_{id}}{2}$	$v_{i2} = v_{icm} - \frac{v_{id}}{2}$
---------------------------------------	---------------------------------------

We solve for the differential output  $v_d$  and the common mode output  $v_{cm}$  separately using different models and then combine the results.

## DIFFERENTIAL MODE ANALYSIS - solving for the differential mode voltage gain $A_d$

<p><b>DM MODEL</b></p>	<p>Since the circuit is symmetrical and the differential mode inputs are <math>180^\circ</math> out of phase, a ground potential results at the emitters. The two halves of the circuit are isolated. Since there is an output only on the right-hand half, this is the only part of the circuit we include in this analysis.</p> $i_e = -\frac{v_{id}}{2} \div r_e = -\frac{v_{id}}{2r_e} \qquad i_c = \frac{\beta}{\beta+1} \left( -\frac{v_{id}}{2r_e} \right)$ $v_{dout} = -i_c R_C = \frac{\beta}{\beta+1} \left( \frac{v_{id}}{2r_e} \right) R_C \qquad A_d = \frac{v_{dout}}{v_{id}}$ <p><math>A_d</math> is the differential mode gain [V/V]</p>
------------------------	--

## COMMON MODE ANALYSIS - solving for the common mode voltage gain $A_{cm}$

<p><b>AC ANALYSIS</b></p>	<p>Because of the symmetry of the circuit, we can write <math>R</math> as two parallel <math>2R</math> resistors and observe that no current flows between them. Therefore this connection can be eliminated and we separate the circuit into halves. Once again, we need only look at the right-hand half since that contains the output.</p> <p>Even though we have looked only at the right-hand side in both phases of the analysis, the presence of the left-hand side does significantly affect the outcome.</p>	<p><b>CM MODEL</b></p>
$i_e = \frac{v_{icm}}{r_e + 2R} \qquad i_c = \frac{\beta}{\beta+1} \left( \frac{v_{icm}}{r_e + 2R} \right) \qquad v_{cmout} = -i_c R_C = \frac{\beta}{\beta+1} \left( \frac{v_{icm}}{2r_e} \right) R_C \qquad A_{cm} = \frac{v_{cmout}}{v_{icm}}$		

## COMMON MODE REJECTION RATIO (CMRR)

$\text{CMRR} = \left  \frac{A_d}{A_{cm}} \right $	$\text{CMRR}_{\text{dB}} = 20 \log_{10} \left  \frac{A_d}{A_{cm}} \right $
---	--