

The SPICE II simulation software package is familiar to most designers working in computer-aided design of integrated circuits. Developed by L. W. Nagel in 1973, SPICE II has become a widely available, well-understood design tool for IC modeling and analysis. But, SPICE II has a shortcoming: its standard simulation programs were developed when all MOSFETs were low-power devices. Power MOS devices are growing in use today, both as discrete components and, potentially, as output stages of power integrated circuits. SPICE II in its current form doesn't recognize these new developments. Its built-in FET models aren't able to simulate all the modes of new power MOS device operation. For example, SPICE II doesn't recognize the way a power MOSFET's internal capacitances change with bias conditions, the presence of a cascode JFET that complicates both static and dynamic operation, or the presence of a parasitic body diode that affects operation in the third quadrant. Without this information, SPICE II will predict power MOSFET performance that is incorrect.

Since SPICE II's internal device models can't be easily changed for all existing copies, we looked for another approach to update the capabilities of this widely used simulation package in its standard form. Adding a "subcircuit" of external components that complement the devices within the SPICE II software, so as to form a true, equivalent circuit of a power MOSFET, is the answer.

The subcircuit works nicely with the standard SPICE II software, providing a model with all the terminal characteristics of a power MOSFET. Parameters of the subcircuit model can be determined from simple terminal measurements or from standard data sheets, using the algorithmic and empirical approach described below. Once these parameters are in place, SPICE II can be used to accurately simulate either p-channel or n-channel power MOSFET devices over a wide range of currents and voltages. The subcircuit functions as an embedded subroutine, so it can be used repetitively for any number of power MOSFETs in a design. This technique can be used to model power MOSFETs with any version of the SPICE II program presently available, without any modifications to its internal source code. The technique can also be used with other commercially available or in-house-developed circuit simulators.

Modeling The Power MOSFET

A cross-sectional view of a cell of a Intersil IRF130 power MOSFET is shown in Figure 1. The easiest way to understand its electrical characteristics is to think of it as a vertical JFET, driven in cascode from a low-voltage lateral MOSFET.^{1, 2} When the gate is positively biased with respect to the n-bulk, an accumulation layer forms in the n-region beneath the gate. This layer acts as the drain of the lateral MOSFET, as well as the source of the vertical JFET. The JFET channel is then-region between the two p-type body diffusions, which act as the gate of the JFET. The JFET drain is the n+ bulk, usually thought of as the power MOSFET drain.

 


FIGURE 1. A CROSS-SECTIONAL VIEW SHOWS THE PHYSICAL MAKEUP OF THE LATERAL LOW-VOLTAGE MOSFET AND VERTICAL JFET THAT OPERATE IN CASCODE AS THE POWER MOSFET.

When you look at the power MOSFET this way, it becomes possible to use the standard SPICE II built-in device models, because SPICE II can simulate both the vertical JFET and the lateral MOSFET. When we use the subcircuit to add the rest of the Intersil IRF130 power MOSFET to these SPICE II-simulated devices, we get a satisfactory equivalent circuit, shown in Figure 2.

The gate-to-source capacitance of the Intersil IRF130 power MOSFET is represented by C_{21} . It is really a composite of two capacitances. The first is formed between the polysilicon gate and source metal (with the thick oxide as a dielectric). The second is formed between the gate and the n+ source (with the thin oxide acting as the dielectric). The value of C_{21} is essentially unchanged by voltage or current.

Capacitor C_{24} is formed between the power MOSFET gate and the accumulation layer, with the thin gate oxide as a dielectric. So long as the gate is positive with respect to the n-neck region, the accumulation layer exists and C_{24} doesn't change. But, if the external drain voltage (less their voltage drop across then-drift region) approaches the gate voltage, the accumulation layer starts to disappear. When that happens, C_{24} abruptly drops in value. This sudden change has to be taken into consideration.

To find the JFET drain resistance, we use the value of source resistance, R_{SOURCE} , and plots of I_{DS} versus V_{DS} for operation in the linear region, as shown in Figure 4.

To find the current, resistance and capacitance parameters of the body diode (D_{BODY} in Figure 2), first plot $\log I_{DS}$ versus V_{DS} , as shown in Figure 5, holding the gate voltage, V_{GS} , negative for third-quadrant operation; i.e., where V_{DS} is less than 0. This plot gives the saturation current and resistance of D_{BODY} . The minority-carrier transit-time parameter (TT) of the SPICE II program is chosen to provide the best fit to measured transient reverse-recovery data. The junction capacitance value of D_{BODY} is equal to the power MOSFET device output capacitance, C_{OSS} , at zero volts. This value can be obtained from the device data sheet, or by bridge measurement. It is usually specified at 25 volts, and may be converted to zero volts by multiplying by 6.

 


FIGURE 3. THIS PLOT OF THE SQUARE ROOT OF DRAIN CURRENT vs. GATE VOLTAGE DEFINES THE THRESHOLD VOLTAGE, V_{TO} , $(K_P/2)^{0.5}$, AND R_{SOURCE} , FOR THE POWER MOSFET.

 


FIGURE 4. DRAIN CURRENT vs. DRAIN VOLTAGE OF THE POWER MOSFET PLOTTED USING CONSTANT GATE VOLTAGES. THIS CURVE DEFINES THE ON RESISTANCE OF THE DEVICE.

 


FIGURE 5. THIS PLOT OF $\log I_D$ VS V_{DS} IN THIRD-QUADRANT OPERATION OF THE POWER MOSFET DEFINES I_S AND R_S , OF THE PARASITIC BODY DIODE, D_{BODY} .

To properly simulate avalanche breakdown voltage with the added clamp circuit (diode D_{BREAK} and voltage source V_{BREAK} in Figure 2), first set the voltage level of V_{BREAK} equal to the measured value of drain breakdown voltage. Then, adjust the SPICE II model parameters I_S , N , and R_S for D_{BREAK} to obtain the best fit to the measured breakdown voltage curve.

Selection of capacitors C_{21} , C_{23} , and C_{24} , and the parameters of the JFET (all shown in Figure 2), can be made using the curves of Figure 6. This is a plot of drain and gate voltage versus time for a power MOSFET driven with constant

 


FIGURE 6. PLOTTING DRAIN AND GATE VOLTAGES OF THE POWER MOSFET VS TIME DETERMINES THE VALUES OF C_{21} , C_{23} , C_{24} , AND V_{pinch} .

gate current (I_G).¹ The initial slope of the V_{GS} curve defines C_{21} (since for any value of gate voltage, V_{GS} , less than threshold voltage, V_{TO} , the power MOSFET is in its off-state, so that the gate-to-source capacitance, C_{21} , charges linearly under constant-current conditions). As V_{TO} is reached, the low-voltage lateral MOSFET (Figure 2) turns on, and its drain voltage drops toward its minimum value.

At the outset, the JFET is operating beyond pinch-off, and the slope of the V_{DS} -versus-time curve is controlled by C_{23} . However, when the drain voltage falls below V_{PINCH} , the JFET conducts, strongly coupling C_{24} to the JFET drain and greatly reducing the drain voltage slew rate. Thus, the value of C_{23} can be approximated from the steep slope of the V_{DS} curve in Figure 6, while the value of $C_{21}+C_{23}+C_{24}$ corresponds to the labelled V_{GS} slope. These values can be adjusted slightly to give the best slope fit. A trial value of V_{PINCH} (and V_{TO}) is given by the labelled intercept of the V_{DS} curve. Adjustments of this value will control the length of the gate plateau voltage needed to complete the curve fit.

Table I lists the preferred algorithm for parameter extraction; Table II summarizes the required empirical inputs. Together, these tables will aid in setting up the parameters for evaluation of a power MOSFET with SPICE II and the subcircuit. As an example, Table 3 summarizes the input parameters for the SPICE II model and subcircuit, determined for the Intersil IRF130 power MOSFET, using the approach just described. The IRF130 is rated at 14 amperes and has a 100-volt blocking capability.

TABLE 1. PREFERRED ALGORITHM FOR PARAMETER EXTRACTION

1.	Determine K_P of lateral MOS
2.	Determine V_{TO} of lateral MOS
3.	Determine C_{21}
4.	Determine $C_{21} + C_{23} + C_{24}$
5.	Determine R_{source} and JFET drain resistance
6.	Assign beta of JFET = 100 x K_P of lateral MOS
7.	Use trial V_{PINCH}
8.	Use trial C_{23} and calculate C_{24}
9.	Curve fit for slope by repeating step 8 with different values of C_{23} .
10.	Adjust V_{PINCH} and V_{TO} of JFET to fix gate-voltage plateau

TABLE 2. EMPIRICAL INPUTS

MOSFET	Enhancement mode: $W = L = 1\mu\text{m}$; K_P (Figure 3); V_{TO} (Figure 3); C 's = 0; $T_{OX} = 1E6\mu\text{m}$
JFET	Depletion mode; area factor = 1; Beta = 100 K_P (Figure 3); $V_{TO} = -V_{pinch}$ (Figure 6); C 's = diode lifetime = 0; diode ideality factor = 1.0; $I_S = 1E - 20$; R_D (Figure 4)
D_{BODY}	I_S from Figure 5; Ideality Factor = 1.0; R_S from Figure 5 (must be very much smaller than R_D); C (from C_{OSS}); lifetime = best fit to T_{RR}

TABLE 2. EMPIRICAL INPUTS (Continued)

D_{BREAK}	$I_S = \text{arbitrary}$; $C = \text{lifetime} = 0$; ideality factor = best low-current fit; $R = \text{best high-current fit}$
D1	$I_S = 1E - 13$; $C = \text{lifetime} = 0$; ideality factor = 0.03; $R_S = 1$
R_{SOURCE}	Figure 3
L_{SOURCE}	Approx. $(5L)\ln(4L/d)$ nH; L and d are source wire inches
V_{PINCH}	Figure 6
V_{BREAK}	Avalanche voltage
C_{21}	Figure 6
C_{23}	Figure 6
C_{24}	Figure 6

TABLE 3 - INPUT PARAMETERS OF IRF130 TO SPICE MODEL

SPICE PARAMETER	INTERSIL IRF130 VALUE
LATERAL MOS	
Model Level	1
T_{OX}	1E06 μm
V_{TO}	3.4V
K_P	6.4A/V ²
W, L	1.0 μm
VERTICAL JFET	
JMOD Area	1
V_{TO}	-6.4V
Beta	640
I_S	10 ⁻²⁰
R_D	42.15 x 10 ⁻³ Ω
D_{BODY}	
CJO	1650pF
IT	70 x 10 ⁻⁹
I_S	3 x 10 ⁻¹²
R_S	2.5 x 10 ⁻³ Ω
PASSIVE ELEMENTS	
C_{21}	900pF
C_{23}	40pF
C_{24}	1360pF
R_{SOURCE}	17.5 x 10 ⁻³ Ω
L_{SOURCE}	7.5 x 10 ⁻⁹ H
V_{BREAK}	117V

Implementing The Subcircuit in SPICE II

Table IV is the input listing for the implementation of the power MOSFET subcircuit in SPICE II software. Nodes are identified for drain, gate, and source of the power MOSFET. The subcircuit then "hooks" to these nodes wherever specified in the SPICE II simulation. Any number of power MOSFETs can be specified. The parameters listed are for an IRF130 power MOSFET.

The Results

The real test of the enhanced SPICE II model is how closely its predicted performance compares with actual measurements. Using the input parameters for the Intersil IRF130 device example given in Table III, we calculated transfer and output curves for the model. These curves were then compared against measured static data. Figures 7 and 8 show the precise fit between predicted and measured static data, even at low values of drain voltage.

To see how the model performs in dynamic prediction, we

simulated first-quadrant operation (including avalanche mode) and third-quadrant operation for the Intersil IRF130 power MOSFET. Once again, the predicted performance of the enhanced SPICE II model fits actual measurements satisfactorily over the entire operating range of the Intersil IRF130, as shown in Figures 9 and 10.

To compare calculated switching performance versus actual measurement on the Intersil IRF130, we used the enhanced SPICE II model to generate switching curves. Figure 11 shows drain and gate voltages versus time with a constant gate-current drive. Figure 12 shows drain and gate voltages.

TABLE 4 - INPUT LISTING OF SUBCIRCUIT MODEL

Listed Parameters Valid for a Intersil IRF130 Power MOSFET

```
* THIS IS THE POWER MOS SUBCIRCUIT
* NODE 3 IS THE POWERMOS DRAIN
* NODE 2 IS THE POWERMOS GATE
* NODE 11 IS THE POWERMOS SOURCE
*
*
.OPTIONS NOMOD NOLIST NOACCT NONODE LIMPTS=250 GMIN=1.0E-20
.SUBCKT POWMOS 3 2 11
C21 2 1 900P
C23 2 3 40P
C24 2 4 1360P
FDSCHRG 4 2 VMEAS 1.0
MOS1 4 2 11 MOSMOD L=1U W=1U
JFET 3 1 4 JMOD AREA=1
DBODY 1 3 DMOD2
RSOURCE 1 10 17.5E-03
LSOURCE 10 11 7.5N
E41 5 11 4 1 1.0
D1 5 6 DMOD
VPINCH 6 8 DC 6.4
VMEAS 8 11 DC 0.0
DBREAK 3 7 DMOD3
VBREAK 7 1 DC 117
.MODEL MOSMOD NMOS VTO=3.4 KP=6.40 TOX=1.0E+06U
.MODEL JMOD NJF VTO=-6.4 BETA=640 IS=1.0E-20 RD=42.5E-03
.MODEL DMOD D IS=1.0E-13 N=0.03 RS=1.0
.MODEL DMOD2 D CJO=1650P TT=70N IS=3.0E-12 RS=2.5E-03
.MODEL DMOD3 D IS=1E-13 RS=2.0 N=1.0
.ENDS
*
*
```

 


FIGURE 7. MEASURED SQUARE ROOT OF DRAIN CURRENT (DRAIN VOLTS = 10) vs. GATE VOLTAGE FOR THE INTERSIL IRF130 POWER MOSFET IS PLOTTED ALONG WITH THE CALCULATED VALUES FOR THE ENHANCED SPICE II MODEL. AN EXCELLENT FIT IS OBTAINED.

 


FIGURE 8. PLOTS OF DRAIN CURRENT vs. DRAIN VOLTAGE FOR THE INTERSIL IRF130 POWER MOSFET SHOW AN EXCELLENT FIT BETWEEN MEASURED VALUES AND THOSE CALCULATED BY THE ENHANCED SPICE II MODEL FOR VARIOUS VALUES OF CONSTANT GATE VOLTAGE.

 


FIGURE 9. FIRST QUADRANT DRAIN CURRENT vs. DRAIN VOLTAGE WITH V_{GS} HELD CONSTANT IS CALCULATED BY THE ENHANCED SPICE II MODEL OF THE INTERSIL IRF130 POWER MOSFET. NOTE THAT THE MODEL PREDICTS AVALANCHE BREAKDOWN.

 


FIGURE 10. THIRD-QUADRANT OPERATION OF THE INTERSIL IRF130 SHOWS AGREEMENT BETWEEN THE PREDICTED VALUES OF THE ENHANCED SPICE II MODEL AND ACTUAL MEASURED VALUED OF DRAIN CURRENT vs DRAIN VOLTAGE AT DIFFERENT VALUED OF CONSTANT GATE VOLTAGE.

 


FIGURE 11. THESE PLOTS OF DRAIN AND GATE VOLTAGES vs. TIME FOR CONSTANT GATE CURRENT SHOW AGREEMENT BETWEEN THE PREDICTIONS OF THE ENHANCED SPICE II MODEL (a) AND MEASURED PERFORMANCE OF THE INTERSIL IRF130 POWER MOSFET (b).

 


FIGURE 12. SWITCHING PERFORMANCE OF THE INTERSIL IRF130 POWER MOSFET IS CLOSELY PREDICTED BY THE ENHANCED SPICE II MODEL IN THIS PLOT OF MEASURED AND CALCULATED VALUES OF DRAIN AND GATE VOLTAGES vs. TIME IN A STANDARD SWITCHING CIRCUIT.

 


FIGURE 13. THE CALCULATED THIRD-QUADRANT DIODE RECOVERY WAVEFORM OF THE ENHANCE SPICE II MODEL SHOWS GOOD AGREEMENT WITH THAT ACTUALLY MEASURED FOR THE INTERSIL IRF130 POWER MOSFET

Finally, the enhanced model was used to compare calculated and measured body diode (D_{BODY} in Figure 2) recovery time curves in third-quadrant operation of the Intersil power MOSFET. Figure 13 shows the good agreement between predicted and actual results.

This approach provides excellent results when there is a need to model the performance of a power MOSFET. Not only will the approach update SPICE II (or other circuit simulation CAD program) so that it will simulate the latest state-of-the-art in MOS power, but it will allow quick analysis of every static and dynamic characteristic for suitability in a proposed design.

References

1. Wheatley, Jr., C.F. and Ronan Jr., H.R., "Switching Waveforms of the L^2 FET: A 5-Volt Gate Drive Power MOSFET," Power Electronic Specialist Conference Record, June 1984, p. 238.
2. Ronan Jr., H.R. and Wheatley Jr., C.F., "Power MOSFET Switching Waveforms: A New Insight," Proceedings of Powercon 11, April 1984, p. C3.

Niehaus, H.A., Bowers, J.C. and Herren Jr., P.C., "A High Power MOSFET Computer Model," Power Conversion International, January 1982, p. 65.

All Intersil semiconductor products are manufactured, assembled and tested under **ISO9000** quality systems certification.

Intersil semiconductor products are sold by description only. Intersil Corporation reserves the right to make changes in circuit design and/or specifications at any time without notice. Accordingly, the reader is cautioned to verify that data sheets are current before placing orders. Information furnished by Intersil is believed to be accurate and reliable. However, no responsibility is assumed by Intersil or its subsidiaries for its use; nor for any infringements of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of Intersil or its subsidiaries.

For information regarding Intersil Corporation and its products, see web site www.intersil.com

Sales Office Headquarters

NORTH AMERICA

Intersil Corporation
P. O. Box 883, Mail Stop 53-204
Melbourne, FL 32902
TEL: (407) 724-7000
FAX: (407) 724-7240

EUROPE

Intersil SA
Mercure Center
100, Rue de la Fusee
1130 Brussels, Belgium
TEL: (32) 2.724.2111
FAX: (32) 2.724.22.05

ASIA

Intersil (Taiwan) Ltd.
7F-6, No. 101 Fu Hsing North Road
Taipei, Taiwan
Republic of China
TEL: (886) 2 2716 9310
FAX: (886) 2 2715 3029